

# Chipper Bootcamp

Jonathan Bachrach




EECS UC Berkeley


July 9, 2015

- introduction to reconfigurable computing
- get you started with Chipper
- get a basic working knowledge of Chipper
- learn how to think in Chipper
- know where to get more information

   
## Register Transfer Level = RTL

- logic and state
- state machines
- e.g., adders and registers
- e.g., counter example:



 

 - what's best machine?
- how to most efficiently implement machine?



would love to go app -> gates but ... it's really hard

\* HLS = High Level Synthesis



- use 10% of energy
- yearly power use of phone == refrigerator
- cost of computing infrastructure is often < yearly energy bill
- only starting to bring world online
- energy is starting to dominate everything!!!
- digital designs yield 100-1000x win in efficiency




- mostly EE backgrounds
- very little PL experience
- efficiency is everything!

- slow hardware design
  - 1980's style languages and baroque tool chains with ad hoc scripts
  - manual optimization obscuring designs
  - minimal compile-time and run-time errors
  - army of people in both CAD tools and design – costs \$10Ms
- slow and expensive to synthesize
  - takes order days
  - not robust and so largely manual process
  - proprietary tools – cost > \$1M / year / seat
- slow testing and evaluation
  - runs 200M x slower than code runs in production
  - army of verification people – costs \$10Ms
- slow and expensive fabrication
  - very labor intensive – costs \$1Ms
- design costs dominate
- very few ASIC designs and chip startups



- had to program in assembly language (or fortran)
- compilation took hours or days
- got minimal compile or run time warnings or errors
- finding bugs took hours or weeks
- burning “CD”s cost \$1Ms

 - Software startups would be rare
- CS enrollment would go way down!




- could build a “chip” in an hour (or a day) \*
  - build and fab tools were low cost (or free) \*
  - could create reusable and abstract modules
  - had large library of standard components to choose from
  - could create chips with small teams
- 
- Hardware startups would be common
  - EE enrollment might go way up!



*\* FPGAs almost fit the bill but tools are painful to use and painfully slow*

- 1 write verilog design structurally – literal
- 2 verilog generate command – limited
- 3 write perl script that writes verilog – awkward
 
```
module counter (clk, reset);  
  input clk;  
  input reset;  
  parameter W = 8;  
  reg [W-1:0] cnt;  
  always @ (posedge clk)  
  begin  
    if (reset)  
      cnt = 0  
    else  
      cnt = cnt + 1  
    end  
endmodule
```




- Classes are provided for circuit components:

- `Register(name)`
- `Adder()`
- `Multiplexor()`
- `Wire(name)`
- `Constant(value)`


and `new` used to construct components and `connect` used to wire them together:

- `new Register(name)`
- `...`
- `connect(input, output)`

```
defn main () :  
  ;; Create Components  
  val reset      = Wire("reset")  
  val counter    = Register("counter")  
  val adder      = Adder()  
  val multiplexor = Multiplexor()  
  val one        = UInt(1)  
  val zero       = UInt(0)  
  
  ;; Connect Components  
  connect(multiplexor.choice, reset)  
  connect(multiplexor.in_a, zero.out)  
  connect(multiplexor.in_b, adder.out)  
  connect(counter.in, multiplexor.out)  
  connect(adder.in_a, counter.out)  
  connect(adder.in_b, one.out)  
  
  ;; Produce Verilog  
  generate_verilog(counter)
```

 


```
defn main () :  
  ;; Create Components  
  val reset      = Wire("reset")  
  val counter    = Register("counter")  
  val adder      = Adder()  
  val multiplexor = Multiplexor()  
  val one        = UInt(1)  
  val zero       = UInt(0)  
  
  ;; Connect Components  
  connect(multiplexor.choice, reset)  
  connect(multiplexor.in_a, zero.out)  
  connect(multiplexor.in_b, adder.out)  
  connect(counter.in, multiplexor.out)  
  connect(adder.in_a, counter.out)  
  connect(adder.in_b, one.out)  
  
  ;; Produce Verilog  
  generate_verilog(counter)
```

 

- using Stanza to programmatically generate hardware
- can use full power of Stanza (loops, arrays, conditionals, ...)
- zero cost abstraction

```
defn main () :  
  ;; Create Components  
  val reset      = Wire("reset")  
  val counter    = Register("counter")  
  val adder      = Adder()  
  val multiplexor = Multiplexor()  
  val one        = UInt(1)  
  val zero       = UInt(0)  
  
  ;; Connect Components  
  connect(multiplexor.choice, reset)  
  connect(multiplexor.in_a, zero.out)  
  connect(multiplexor.in_b, adder.out)  
  connect(counter.in, multiplexor.out)  
  connect(adder.in_a, counter.out)  
  connect(adder.in_b, one.out)  
  
  ;; Produce Verilog  
  generate_verilog(counter)
```

 

■ but Stanza is pretty Verbose, how can we do better?

```
defn main () :  
  ;; Create Components  
  val reset      = Wire("reset")  
  val counter    = Register("counter")  
  val adder = Adder()  
  val multiplexor = Multiplexor()  
  val one        = UInt(1)  
  val zero       = UInt(0)  
  
  ;; Connect Components  
  connect(multiplexor.choice, reset)  
  connect(multiplexor.in_a, zero.out)  
  connect(multiplexor.in_b, adder.out)  
  connect(counter.in, multiplexor.out)  
  connect(adder.in_a, counter.out)  
  connect(adder.in_b, one.out)  
  
  ;; Produce Verilog  
  generate_verilog(counter)
```



```
defn main () :  
  ;; Create Components  
  val reset      = Wire("reset")  
  val counter    = Register("counter")  
  val multiplexor = Multiplexor()  
  val one        = UInt(1)  
  val zero       = UInt(0)  
  
  ;; Connect Components  
  connect(multiplexor.choice, reset)  
  connect(multiplexor.in_a, zero.out)  
  connect(multiplexor.in_b,  
    make_adder(one.out, counter.out))  
  connect(counter.in, multiplexor.out)  
  
  ;; Produce Verilog  
  generate_verilog(counter)
```

*functional programming*



```
defn main () :  
  ;; Create Components  
  val reset      = Wire("reset")  
  val counter    = Register("counter")  
  val multiplexor = Multiplexor()  
  val one        = UInt(1)  
  val zero       = UInt(0)  
  
  ;; Connect Components  
  connect(multiplexor.choice, reset)  
  connect(multiplexor.in_a, zero.out)  
  connect(multiplexor.in_b,   
          make_adder(one.out, counter.out))  
  connect(counter.in, multiplexor.out)  
  
  ;; Produce Verilog  
  generate_verilog(counter)
```



```
defn main () :  
  ;; Create Components  
  val reset      = Wire("reset")  
  val counter    = Register("counter")  
  val one        = UInt(1)  
  val zero       = UInt(0)  
  
  ;; Connect Components  
  connect(counter.in,  
    make_multiplexor(reset,  
      zero.out  
    make_adder(one.out, counter.out)))  
  
  ;; Produce Verilog  
  generate_verilog(counter)
```

*functional programming*

```
defn main () :  
  ;; Create Components  
  val reset = Wire("reset")  
  val counter = Register("counter")  
  val one = UInt(1)  
  val zero = UInt(0)  
  
  ; Connect Components  
  connect(counter.in,  
    make_muxplexor(reset,  
      zero.out ,  
      make_adder(one.out , counter.out)))  
  
  ;; Produce Verilog  
  generate_verilog(counter)
```



```
defn main () :  
  ;; Create Components  
  val reset = Wire("reset")  
  val counter = Register("counter")  
  
  ;; Connect Components  
  connect(counter.in,  
    make_muxplexor(reset,  
      UInt(0) ,  
      make_adder(UInt(1) , counter.out)))  
  
  ;; Produce Verilog  
  generate_verilog(counter)
```

*functional programming*

```
defn main () :  
  ;; Create Components  
  val reset = Wire("reset")  
  val counter = Register("counter")  
  
  ;; Connect Components  
  connect(counter.in,  
    make_muxplexor(reset,  
      UInt(0),  
      make_adder(UInt(1), counter.out) ))  
  
  ;; Produce Verilog  
  generate_verilog(counter)
```



```
defn main () :  
  ;; Create Components  
  val reset = Wire("reset")  
  val counter = Register("counter")  
  
  ;; Connect Components  
  connect(counter.in,  
    make_muxplexor(reset,  
      UInt(0),  
      UInt(1) + counter.out ))  
  
  ;; Produce Verilog  
  generate_verilog(counter)
```

**operator overloading**

```
defn main () :  
  ;; Create Components  
  val reset = Wire("reset")  
  val counter = Register("counter")  
  
  ;; Connect Components  
  connect(counter.in,  
    make_muxplexor(reset,  
      UInt(0),  
      UInt(1) + counter.out) )  
  
  ;; Produce Verilog  
  generate_verilog(counter)
```



```
defn main () :  
  ;; Create Components  
  val reset = Wire("reset")  
  val counter = Register("counter")  
  
  ;; Connect Components  
  counter.in :=  
    make_muxplexor(reset,  
      UInt(0),  
      UInt(1) + counter.out)  
  
  ;; Produce Verilog  
  generate_verilog(counter)
```

**operator overloading**

```
defn main () :  
  ;; Create Components  
  val reset = Wire("reset")  
  val counter = Register("counter")  
  
  ;; Connect Components  
  counter.in :=  
    make_mux(reset,  
      UInt(0),  
      UInt(1) + counter.out )  
  
  ;; Produce Verilog  
  generate_verilog(counter)
```



```
defn main () :  
  ;; Create Components  
  val reset = Wire("reset")  
  val counter = Register("counter")  
  
  ;; Connect Components  
  when reset :  
    counter.in := UInt(0)  
  else :  
    counter.in := UInt(1) + counter.out  
  
  ;; Produce Verilog  
  generate_verilog(counter)
```

**dynamic scoping, closures, object-orientation**

```
defn main () :  
  ;; Create Components  
  val reset = Wire("reset") \colorbox{red}{val  
    counter = Register("counter")}  
  
  ;; Connect Components  
  when reset :  
    counter.in := UInt(0)  
  else :  
    counter.in := UInt(1) + counter.out  
  
  ;; Produce Verilog  
  generate_verilog(counter)
```



```
defn main () :  
  ;; Create Components  
  wire reset : UInt  
  reg counter : UInt  
  
  ;; Connect Components  
  when reset :  
    counter.in := UInt(0)  
  else :  
    counter.in := UInt(1) + counter.out  
  
  ;; Produce Verilog  
  generate_verilog(counter)
```

## introspection

```
defn main () :  
  ;; Create Components  
  wire reset : UInt  
  reg counter : UInt  
  
  ;; Connect Components  
  when reset :  
    counter.in := UInt(0)  
  else :  
    counter.in := UInt(1) + counter.out  
  
  ;; Produce Verilog  
  generate_verilog(counter)
```



```
defn make_counter(reset: UInt) :  
  reg counter : UInt  
  when reset :  
    counter.in := UInt(0)  
  else :  
    counter.in := UInt(1) + counter.out  
  counter  
}  
  
defn main () :  
  ;; Create Components  
  wire reset : UInt  
  wire counter = make_counter(reset)  
  
  ;; Produce Verilog  
  generate_verilog(counter)
```

*functional programming*

```
defn make_counter( reset: UInt ) :  
  reg counter : UInt  
  when reset :  
    counter.in := UInt(0)  
  else :  
    counter.in := UInt(1) + counter.out  
  counter  
  
defn main () :  
  ;; Create Components  
  wire reset : UInt  
  wire counter = make_counter( reset )  
  
  ;; Produce Verilog  
  generate_verilog(counter)
```




```
defn make_counter() :  
  reg counter : UInt  
  when reset :  
    counter.in := UInt(0)  
  else :  
    counter.in := UInt(1) + counter.out  
  counter  
  
defn main () :  
  ;; Create Components  
  val reset = Wire()  
  val counter =  
    withReset(reset):  
      make_counter()  
  ;; Produce Verilog  
  generate_verilog(counter)
```

 **dynamic scoping**



```
def make_counter() = {  
  reg counter : UInt  
  when reset :  
    counter.in := UInt(0)  
  else :  
    counter.in := UInt(1) + counter.out  
  counter  
}  
  
defn main () :  
  ;; Create Components  
  wire reset : UInt  
  wire counter =  
    withReset(reset) :  
      make_counter(reset)  
  ;; Produce Verilog  
  generate_verilog(counter)
```



- every construct actually creates a concrete circuit
- know cost of everything
- layered and can choose level of abstraction
- not “stanza to hardware” compiler

## Crucial

- Type Inference
- Infix Operator Overloading
- Lightweight Closures
- Dynamic Scoping
- Introspection ( or Simple Macros )
- Functional Programming

## Even Better with

- Object Orientation
- Powerful Macros

- Install VirtualBox
- File->Import appliance, chipper-vm.ova
- Start
- Login (username: chipper-bootcamp, password: chipper)
- GTKWave, Emacs, etc. all installed

```
cd chipper-tutorial  
git pull  
git submodule update
```


```
chipper-tutorial/  
  Makefile  
  generated/  
    examples/  
    problems/  
    solutions/  
examples/  # Contains chipper examples  
  Makefile  
  FullAdder.stanza ...  
problems/  # Contains skeletal files for tutorial problems  
  Makefile  
  Accumulator.stanza ...  
solutions/ # Contains solutions to problems  
  Makefile  
  Counter.stanza ...
```

```
cd $TUT_DIR  
make
```

If your system is set up correctly, you should see a message [success] followed by the total time of the run, and date and time of completion.

```
open chipper-tutorial/chipper/doc/bootcamp/bootcamp.pdf
```

 - A hardware construction language
  - “synthesizable by construction”
  - creates graph representing hardware
- Embedded within Stanza language to leverage mindshare and language design
- Best of hardware and software design ideas
- Multiple targets
  - Simulation and synthesis
  - Memory IP is target-specific
- **Not Stanza app -> Verilog arch**






- Object Oriented
  - Factory Objects, Classes
  - Traits, overloading etc
  - Strongly typed with type inference
- Functional
  - Higher order functions
  - Anonymous functions
  - Currying etc
- Extensible
  - Macro System
  - Domain Specific Languages (DSLs)
- Fast
  - Cooperative Coroutine System
  - Native Optimizing Compiler


\*\* Invented by Patrick Li @ EECS Berkeley

<http://www.lbstanza.org>


`mux(x > y, x, y)`

 
 
```
defmodule Max2 :  
  input x : UInt<8>  
  input y : UInt<8>  
  output z : UInt<8>  
  io.z := mux(io.x > io.y, io.x, io.y)
```



 
```
inst m1 : Max2()  
m1.x := a  
m1.y := b  
inst m2 : Max2()  
m2.x := c  
m2.y := d  
inst m3 : Max2()  
m3.x := m1.z  
m3.y := m2.z
```




```
defn max2 (x, y): mux(x > y, x, y)
```


```
max2(x, y)
```

 
 
```
defmodule MaxN (n: Int, w: Int) :  
  input in : UInt<w>[4]  
  output out : UInt<w>  
  out := reduce(max2, in)
```


 
```
defmodule GCD :  
  input a      : UInt<16>  
  input b      : UInt<16>  
  output z     : UInt<16>  
  output valid  : UInt<1>  
  reg x = a  
  reg y = b  
  when x > y :  
    x := x - y  
  else :  
    y := y - x  
  z := x  
  valid := y == UInt(0)
```



```
cd ~/chipper-tutorial/examples  
make GCD.out
```

```
...  
PASSED  
[success] Total time: 2 s, completed Feb 28, 2013 8:14:37 PM
```




```
cd ~/chipper-tutorial/examples  
make GCD.v
```

The Verilog source is roughly divided into three parts:

- 1 Module declaration with input and outputs
- 2 Temporary wire and register declaration used for holding intermediate values
- 3 Register assignments in `always @ (posedge clk)`

```
defmodule FullAdder :  
  input a: UInt<1>  
  input b: UInt<1>  
  input cin: UInt<1>  
  output sum: UInt<1>  
  output cout: UInt<1>  
  ;; Generate the sum  
  wire a_xor_b = a ^ b  
  sum := a_xor_b ^ io.cin  
  ;; Generate the carry  
  wire a_and_b = a & b  
  wire b_and_cin = b & cin  
  wire a_and_cin = a & cin  
  cout := a_and_b |  
    b_and_cin | a_and_cin
```

 

```
defmodule FullAdder :  
  input a: UInt<1>  
  input b: UInt<1>  
  input cin: UInt<1>  
  output sum: UInt<1>  
  output cout: UInt<1>  
  ;; Generate the sum  
  wire a_xor_b = a ^ b  
  sum := a_xor_b ^ io.cin  
  ;; Generate the carry  
  wire a_and_b = a & b  
  wire b_and_cin = b & cin  
  wire a_and_cin = a & cin  
  cout := a_and_b |  
    b_and_cin | a_and_cin
```

```
module FullAdder(  
  input io_a,  
  input io_b,  
  input io_cin,  
  output io_sum,  
  output io_cout);  
  wire T0;  
  wire a_and_cin;  
  wire T1;  
  wire b_and_cin;  
  wire a_and_b;  
  wire T2;  
  wire a_xor_b;  
  
  assign io_cout = T0;  
  assign T0 = T1 | a_and_cin;  
  assign a_and_cin = io_a & io_cin;  
  assign T1 = a_and_b | b_and_cin;  
  assign b_and_cin = io_b & io_cin;  
  assign a_and_b = io_a & io_b;  
  assign io_sum = T2;  
  assign T2 = a_xor_b ^ io_cin;  
  assign a_xor_b = io_a ^ io_b;  
endmodule
```


```
defmodule FullAdder :  
  input a: UInt<2>  
  input b: UInt<2>  
  input cin: UInt<2>  
  output sum: UInt<2>  
  output cout: UInt<1>  
  ;; Generate the sum  
  wire a_xor_b = a ^ b  
  sum := a_xor_b ^ io.cin  
  ;; Generate the carry  
  wire a_and_b = a & b  
  wire b_and_cin = b & cin  
  wire a_and_cin = a & cin  
  cout := a_and_b | b_and_cin |  
    a_and_cin
```

```
module FullAdder(  
  input [1:0] io_a,  
  input [1:0] io_b,  
  input [1:0] io_cin,  
  output [1:0] io_sum,  
  output [1:0] io_cout);  
  wire [1:0] T0;  
  wire [1:0] a_and_cin;  
  wire [1:0] T1;  
  wire [1:0] b_and_cin;  
  wire [1:0] a_and_b;  
  wire [1:0] T2;  
  wire [1:0] a_xor_b;  
  
  assign io_cout = T0;  
  assign T0 = T1 | a_and_cin;  
  assign a_and_cin = io_a & io_cin;  
  assign T1 = a_and_b | b_and_cin;  
  assign b_and_cin = io_b & io_cin;  
  assign a_and_b = io_a & io_b;  
  assign io_sum = T2;  
  assign T2 = a_xor_b ^ io_cin;  
  assign a_xor_b = io_a ^ io_b;  
endmodule
```

```
// clock the new reg value on every cycle  
wire y = x  
reg z := y
```


```
// clock the new reg value when the condition a > b  
reg x : UInt  
when a > b :  
    x := y  
else when b > a :  
    x := z  
else :  
    x := w
```
 
```
defmodule ShiftRegister :  
  input in : UInt<1>  
  output out : UInt<1>  
  reg r0 := in  
  reg r1 := r0  
  reg r2 := r1  
  reg r3 := r2  
  out := r3
```



```
module ShiftRegister(input clk, input reset,  
  input io_in,  
  output io_out);  
  
  reg[0:0] r3;  
  reg[0:0] r2;  
  reg[0:0] r1;  
  reg[0:0] r0;  
  
  assign io_out = r3;  
  always @(posedge clk) begin  
    r3 <= r2;  
    r2 <= r1;  
    r1 <= r0;  
    r0 <= io_in;  
  end  
endmodule
```
 
```
defmodule ShiftRegister :  
  input in : UInt<1>  
  input shift : UInt<1>  
  output out : UInt<1>  
  
  reg r0 : UInt<1>  
  reg r1 : UInt<1>  
  reg r2 : UInt<1>  
  reg r3 : UInt<1>  
  
  when shift :  
    r0 := in  
    r1 := r0  
    r2 := r1  
    r3 := r2  
  out := r3
```



```
defmodule EnableShiftRegister :  
  input in : UInt<1>  
  input shift : UInt<1>  
  output out : UInt<1>  
  
  ;; Register reset to zero  
  reg r0 = UInt<1>(0)  
  reg r1 = UInt<1>(0)  
  reg r2 = UInt<1>(0)  
  reg r3 = UInt<1>(0)  
  
  when shift :  
    r0 := in  
    r1 := r0  
    r2 := r1  
    r3 := r2  
  out := r3
```



## inferred width

```
UInt(1)           ;; decimal 1-bit literal from Stanza Int.
UInt("ha")        ;; hexadecimal 4-bit literal from string.
UInt("o12")        ;; octal 4-bit literal from string.
UInt("b1010")      ;; binary 4-bit literal from string.
```

## specified widths

```
UInt("h_dead_beef") ;; 32-bit literal of type UInt.
UInt(1)              ;; decimal 1-bit literal from Stanza Int.
UInt<8>("ha")         ;; hexadecimal 8-bit literal of type UInt.
UInt<6>("o12")         ;; octal 6-bit literal of type UInt.
UInt<12>("b1010")     ;; binary 12-bit literal of type UInt.
UInt<8>(5)            ;; unsigned decimal 8-bit literal of type UInt.
```

# Sequential Circuit Problem – Accumulator.stanza 49

- write sequential circuit that sums `in` values
- in `chipper-tutorial/problems/Accumulator.stanza`
- run `make Accumulator.out` until passing

```
defmodule Accumulator :  
  input in : UInt<1>  
  output out : UInt<8>  
  
  ;; flush this out ...  
  
  out := UInt(0)
```

```
defmodule BasicALU :
  input a      : UInt<4>
  input b      : UInt<4>
  input opcode : UInt<4>
  output out = UInt<4>
  out := UInt(0)
  when opcode === UInt(0) :
    out := a                ;; pass A
  else when opcode === UInt(1) :
    out := b                ;; pass B
  else when: opcode === UInt(2) :
    out := a + UInt(1)      ;; inc A by 1
  else when: opcode === UInt(3) :
    out := a - UInt(1)      ;; dec B by 1
  else when: opcode === UInt(4) :
    out := a + UInt(4)      ;; inc A by 4
  else when: opcode === UInt(5) :
    out := a - UInt(4)      ;; dec A by 4
  else when: opcode === UInt(6) :
    out := a + b            ;; add A and B
  else when: opcode === UInt(7) :
    out := a - b            ;; sub B from A
  else when: opcode === UInt(8) :
    out := (a < b)          ;; set on A < B
  else :
    out := (a === b)        ;; set on A == B
```

- wire `io.output` defaulted to 0 and then
- conditionally reassigned to based on opcode
- unlike registers, wires are required to be defaulted
- wires also allow forward declarations

Symbol	Operation
+	Add
-	Subtract
*	Multiply
/	UInt Divide
%	Modulo
~	Bitwise Negation
^	Bitwise XOR
& Bitwise AND	UInt
	Bitwise OR
===	Equal
!==	Not Equal
>	Greater
<	Less
>=	Greater or Equal
<=	Less or Equal

```
;; extracts the x through y bits of value  
wire x_to_y = value[x, y]
```

```
;; extract the x-th bit from value  
wire x_of_value = value[x]
```

```
defmodule ByteSelector :  
  input in: UInt<32>  
  input offset: UInt<2>  
  output out: UInt<8>  
  
  when offset === UInt(0) :  
    out := in[7,0]  
  else when offset === UInt(1) :  
    out := in[15, 8]  
  else when offset === UInt(2) :  
    out := in[23,16]  
  else :  
    out := in[31,24]
```

You concatenating bits using Cat:


```
wire A    : UInt<32>
wire B    : UInt<32>
wire bus = cat(A, B) ;; concatenate A and B
```

and replicate bits using Fill:

```
// Replicate a bit string multiple times.
val usDebt = Fill(3, UInt("hA"))
```

```
defmodule LFSR16 :  
  input inc : UInt<1>  
  output out : UInt<16>  
  ;; ...  
  out := UInt(0)
```

 - reg, cat, extract, ^
- init reg to 1
- updates when inc asserted





```
defmodule HiLoMultiplier :  
  input A  : UInt<16>  
  input B  : UInt<16>  
  output Hi : UInt<16>  
  output Lo : UInt<16>  
  wire mult = A * B  
  Lo := mult[15, 0]  
  Hi := mult[31, 16]
```

```
module HiLoMultiplier(  
  input [15:0] io_A,  
  input [15:0] io_B,  
  output[15:0] io_Hi,  
  output[15:0] io_Lo);  
  
  wire[15:0] T0;  
  wire[31:0] mult; // inferred as 32 bits  
  wire[15:0] T1;  
  
  assign io_Lo = T0;  
  assign T0 = mult[4'hf:1'h0];  
  assign mult = io_A * io_B;  
  assign io_Hi = T1;  
  assign T1 = mult[5'h1f:5'h10];  
endmodule
```

Operation	Result Bit Width
$Z = X + Y$	$\max(\text{Width}(X), \text{Width}(Y))$
$Z = X - Y$	$\max(\text{Width}(X), \text{Width}(Y))$
$Z = X \& Y$	$\min(\text{Width}(X), \text{Width}(Y))$
$Z = X   Y$	$\max(\text{Width}(X), \text{Width}(Y))$
$Z = X \wedge Y$	$\max(\text{Width}(X), \text{Width}(Y))$
$Z = \sim X$	$\text{Width}(X)$
$Z = \text{mux}(C, X, Y)$	$\max(\text{Width}(X), \text{Width}(Y))$
$Z = X * Y$	$\text{Width}(X) + \text{Width}(Y)$
$Z = X \ll n$	$\text{Width}(X) + n$
$Z = X \gg n$	$\text{Width}(X) - n$
$Z = \text{cat}(X, Y)$	$\text{Width}(X) + \text{Width}(Y)$
$Z = \text{fill}(n, x)$	$\text{Width}(X) + n$


The Chipper Bool is used to represent the result of logical expressions:

```
wire change = io.a == io.b ;; change gets Bool type
when change : ;; execute if change is true
...
```


You can instantiate a Bool value like this:

```
wire true_value = UInt(true)
wire false_value = UInt(false)
```

- SInt is a signed integer type

 
 
```
defbundle MyFloat :  
  output sign : UInt<1>  
  output exponent : UInt<8>  
  output significand : UInt<23>  
  
wire x : MyFloat  
wire xs = x.sign
```




## Data object with directions assigned to its members


```
defbundle Decoupled :  
  output data : UInt<32>  
  output valid : UInt<1>  
  input ready : UInt<1>
```
 
## Direction assigned at instantiation time

```
defbundle ScaleIO :  
  input in : MyFloat  
  input scale : MyFloat  
  output out : MyFloat
```



```
;; A 4-bit adder with carry in and carry out
defmodule Adder4:
  input A : UInt<4>
  input B : UInt<4>
  input Cin : UInt<1>
  output Sum : UInt<4>
  output Cout : UInt<1>
  ;; Adder for bit 0
  inst Adder0 : FullAdder
  Adder0.a := A[0]
  Adder0.b := B[0]
  Adder0.cin := Cin
  wire s0 = Adder0.sum
  ;; Adder for bit 1
  inst Adder1 = FullAdder
  Adder1.a := A[1]
  Adder1.b := B[1]
  Adder1.cin := Adder0.cout
  wire s1 = Cat(Adder1.sum, s0)
  ...
  ;; Adder for bit 3
  inst Adder3 : FullAdder
  Adder3.a := A[3]
  Adder3.b := B[3]
  Adder3.cin := Adder2.cout
  Sum := Cat(Adder3.sum, s2)
  Cout := Adder3.cout
```

 

- inherits from Module class,
- contains an interface stored in a port field named io, and
- wires together subcircuits in its constructor.

## constructing vecs

```
wire myVec1 : <data type>[<number of elements>]  
wire myVec2 = Vec(<elt0>, <elt1>, ...)
```

## creating a vec of wires

```
wire ufix5_vec10 : UInt<5>[10]
```

## creating a vec of regs

```
reg reg_vec32 : UInt<16>[32]
```

## writing

```
reg_vec32[1] := UInt(0)
```

## reading

```
wire reg5 = reg_vec[5]
```



- add loadability to shift register
- change interface to use vec's

```
defmodule VecShiftRegister :  
  input ins: UInt<w>[4]  
  input load: UInt<1>  
  input shift: UInt<1>  
  output out: UInt<w>  
  
  reg delays: UInt<w>[4]  
  when load :  
    ;; fill in here ...  
  else when shift :  
    ;; fill in here ...  
  out := delays[3]
```

```
class ByteSelector extends Module {
  input in: UInt<32>
  input offset: UInt<2>
  output out: UInt<8>
  out := UInt<8>(0)
  ...


  defn bs-tests () :
    with-tester [t, c] = ByteSelector() :
      val test_in = 12345678
      for i in 0 to 4 all? :
        poke(t, c.in, test_in)
        poke(t, c.offset, t)
        step(1)
      val ref_out = (test_in >> (t * 8)) & 255
      expect(t, c.out, ref_out)
```

```
defclass Tester
defn Tester (dut:String) -> Tester
defmulti dut (t:Tester) -> String
defmulti reset (t:Tester, n:Int) -> Int
defmulti step (t:Tester, n:Int) -> Int
defmulti peek (t:Tester, data:Bits) -> Int
defmulti peek (t:Tester, data:Bits, index:Int) -> Int
defmulti poke (t:Tester, data:Bits, x:Int) -> Int
defmulti poke (t:Tester, data:Bits, i:Int, x:Int) -> Int
defmulti expect (t:Tester, data:Bits, target:Int) -> True|False
defn expect (good:Boolean, msg: Streamable) -> True|False

defn int(x: Boolean) -> BigInt
defn int(x: Int) -> BigInt
defn int(x: Bits) -> BigInt
```

which binds a tester to a module and allows users to write tests using the given debug protocol. In particular, users utilize:

 - **poke** to set input port and state values,
- **step** to execute the circuit one time unit,
- **peek** to read port and state values, and
- **expect** to compare peeked circuit values to expected arguments.



```
> cd chipper-tutorial/examples
> make ByteSelector.out
STARTING ../emulator/problems/ByteSelector
---
RESET 1 -> 1
STARTING TESTS
WIRE-POKE ByteSelector.in = 16807 -> ok
WIRE-POKE ByteSelector.offset = 1 -> ok
STEP 1 -> 0
WIRE-PEEK ByteSelector.out -> 0x41
EXPECT ByteSelector.out VALUE 65 -> 65
WIRE-POKE ByteSelector.in = 548908249 -> ok
WIRE-POKE ByteSelector.offset = 2 -> ok
STEP 1 -> 0
...
WIRE-PEEK ByteSelector.out -> 0x35
EXPECT ByteSelector.out VALUE 53 -> 53
WIRE-POKE ByteSelector.in = 881157273 -> ok
WIRE-POKE ByteSelector.offset = 2 -> ok
STEP 1 -> 0
WIRE-PEEK ByteSelector.out -> 0x85
EXPECT ByteSelector.out VALUE 133 -> 133
SUCCESS
[success] Total time: 26 s, ...
```

In particular, users utilize:

- `poke` to set input port and state values,
- `step` to execute the circuit one time unit,
- `peek` to read port and state values, and
- `expect` to compare peeked circuit values to expected arguments.

## ■ write a testbench for MaxN

```
defmodule MaxN (n: Int, w: Int) :  
  input ins : UInt<w>[n]  
  output out : UInt<w>  
  defn Max2 (x: UInt, y: UInt) :  
    mux(x > y, x, y)  
  out := ins.reduce(Max2)
```

```
;; returns random int in 0..lim-1  
val x = rnd.nextInt(lim)
```

```
defn MaxNTests () :  
  with-tester [t,c] = MaxN() :  
    for i in 0 to 10 do :  
      for j in 0 to num(c) do :  
        ;; FILL THIS IN HERE  
        poke(t, c.ins[0], 0)  
        ;; FILL THIS IN HERE  
      step(1)  
    expect(t, c.out, 1)
```

```
defmodule MemorySearch (inits:Streamable<Int>) :  
  input isRd:   UInt<1>  
  input data:   UInt<4>  
  output done:  UInt<1>  
  output rdAddr: UInt<3>  
  
  wire vals: UInt<4>[7]  
  for (e in inits, i in 0 to false) do:  
    vals[i] := UInt(e)  
  reg index : UInt<4>  
  wire elt   = vals[index]  
  wire isDone = ! isRd & ((elt === data) | (index === UInt(7)))  
  when isRd :  
    index := UInt(0)  
  else when ! isDone :  
    index := index + UInt(1)  
  done := isDone  
  rdAddr := index
```


RAM is supported using the `cmem` construct

```
cmem m : UInt<32>[32]
```

where

- writes to Mems are positive-edge-triggered
- reads are either combinational or positive-edge-triggered
- ports are created by applying a `UInt` index
 
```
cmem regs : UInt<32>[32]  
when wrEn :  
    regs[wrAddr] := wrData  
wire iDat = regs[iAddr]  
wire mDat = regs[mAddr]
```






```
defmodule DynamicMemorySearch (n:Int, w:Int) :  
  input  isWr:   UInt<1>  
  input  wrAddr: UInt<sizeof(w)>  
  input  isRd:   UInt<1>  
  input  data:   UInt<w>  
  output done:   UInt<1>  
  output rdAddr: UInt<sizeof(w)>  
  
  reg index = UInt<sizeof(w)>(0)  
  ;; ...  
  wire elt  = vals[index]  
  wire isDone = ! (isRd | isWr) & ((elt === data) | (index === UInt(n - 1)))  
  when isWr :  
    vals[wrAddr] := data  
  ;; ...  
  else when ! isDone :  
    index := index + UInt(1)  
  done    := isDone  
  rdAddr  := index
```

Sequential read ports are created using sequential memories:

- reads are delayed one cycle
 
```
smem ram1rlw : UInt<32>[1024]  
when wen: ram1rlw[waddr] := wdata  
when ren: eg_raddr := raddr  
wire rdata = ram1rlw[reg_raddr]
```



```
defmodule Stack (n:Int) :  
  input push: UInt<1>  
  input pop: UInt<1>  
  input en: UInt<1>  
  input dataIn: UInt<32>  
  output dataOut: UInt<32>  
  cmem stack_mem : UInt<32>[n] ;; declare stack memory  
  reg sp : UInt<sizeof(n)> sp := UInt(0)  
  wire out : UInt<32> out := UInt(0)  
  when en :  
    ;; Push condition - make sure stack isn't full  
    when push & (sp < UInt(depth)) :  
      stack_mem[sp] := dataIn  
      sp := sp + UInt(1)  
    ;; Pop condition - make sure the stack isn't empty  
    else when pop & (sp > UInt(0)) :  
      sp := sp - UInt(1)  
    when sp > UInt(0) :  
      out := stack_mem[sp - UInt(1)]  
  dataOut := out
```

```


;; A n-bit adder with carry in and carry out
defmodule Adder (n: Int) :
  input A : UInt<n>
  input B : UInt<n>
  input Cin : UInt<1>
  output Sum : UInt<n>
  output Cout : UInt<1>

  ;; create a vector of FullAdders
  inst FAs : FullAdder[n]
  wire carry = UInt<1>[n + 1]
  wire sum = UInt<1>[n]

  ;; first carry is the top level carry in
  carry[0] := Cin

  ;; wire up the ports of the full adders
  for i in 0 to n do :
    FAs[i].a := A[i]
    FAs[i].b := B[i]
    FAs[i].cin := carry[i]
    carry[i + 1] := FAs[i].cout
    sum[i] := FAs[i].sum
  Sum := to-uint(sum)
  Cout := carry[n]


```

 

- write 16x16 multiplication table using Vec

```
defmodule Mul :  
  input x : UInt<4>  
  input y : UInt<4>  
  output z : UInt<8>  
  wire tab : UInt<8>[256]  
  
  ;; TODO: would like to do uint/cat here  
  for i in 0 to 16 do :  
    for j in 0 to 16 do :  
      tab[(i << 4) | j] := UInt(i * j)  
  
  z := tab[cat(x, y)]
```
 
```
defbundle Valid<T> :  
  output data : T  
  output valid : UInt<1>  
  
defmodule GCD :  
  input a : UInt<16>  
  input b : UInt<16>  
  output out : Valid<UInt<16>>  
  ...  
  out.data := x  
  out.valid := y == UInt(0)
```



<b>Bits Properities</b>	log2Up, log2Down, isPow2, PopCount
<b>Numeric Utilities</b>	LFSR16, Reverse, FillInterleaved
<b>Stateful Functions</b>	ShiftRegister, Counter
<b>Priority Encoding Functions</b>	UIntTo0H, 0HToUInt, Mux1H
<b>Priority Encoders</b>	PriorityEncoder, PriorityEncoder0H
<b>Queues and Pipes</b>	Decoupled, Queue, Valid, Pipe
<b>Arbiters</b>	ArbiterIO, Arbiter, RRArbiter

- Required parameter entries controls depth
- The width is determined from the inputs.

```
defbundle QueueIO<T> (entries: Int) :  
  input enq      : DecoupledIO<T>  
  output deq     : DecoupledIO<T>  
  output count   : UInt<log2Up(entries + 1)>
```

```
defmodule Queue<T>  
  (entries: Int,  
   pipe: Boolean = false,  
   flow: Boolean = false  
   flushable: Boolean = false)
```

```
inst q : Queue<UInt>(16)  
q.enq := producer.out  
consumer.in := q.deq
```



directory structure

```
Hello/  
  Hello.stanza # your source file
```

```
defmodule Hello :  
  output out : UInt<8> }  
  out := UInt(33)  
  
defn hello-tests () :  
  with-tester [t,c] = Hello() :  
    step(t, 1)  
    expect(t, c.out, 33)  
  
defn main () :  
  if cmdline-arguments[1] == "--testing" :  
    hello-tests(inst-of Hello)  
  else :  
    println(circuit-of Hello)  
  
defn main () :  
  chipper-main(  
    if cmdline-arguments[1] == "--testing" :  
      hello-tests(inst-of Hello)  
    else :  
      println(circuit-of Hello)
```

## Producing C++

```
chipperc Hello.stanza
```

## Producing Verilog

```
chipperv Hello.stanza
```

## Running the Chipper Tests

```
chipperc Hello.stanza  
Hello "--testing"
```

set hello project up

```
cd ~  
mkdir hello  
cp -r ~/chipper-tutorial/hello/* hello  
cd hello  
sbt run
```

make a change

- make output a function of an new input

`figs/chipper-workflow.pdf`